CODE: 20EST101 SET-1

## ADITYA INSTITUTE OF TECHNOLOGY AND MANAGEMENT, TEKKALI (AUTONOMOUS)

I B.Tech II Semester Supplementary Examinations, October-2022

### BASIC ELECTRICAL ENGINEERING (Common to ME, CSE, AIML & IT)

Time: 3 Hours Max Marks: 60

Answer ONE Question from each Unit All Questions Carry Equal Marks All parts of the Question must be answered at one place

### **UNIT-I**


1. a) State and explain KVL and KCL

5M


b) Explain the source transformation used in electrical network 5M with suitable examples.

(OR)

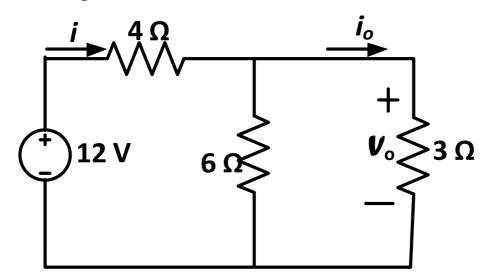- 2. a) Explain about the Ideal and Practical Voltage sources with 5M neat circuit diagrams.
  - b) Find  $v_o$  and  $i_o$  in the circuit shown in below Fig. Calculate the 5M power dissipated in the  $3\Omega$  resistor.



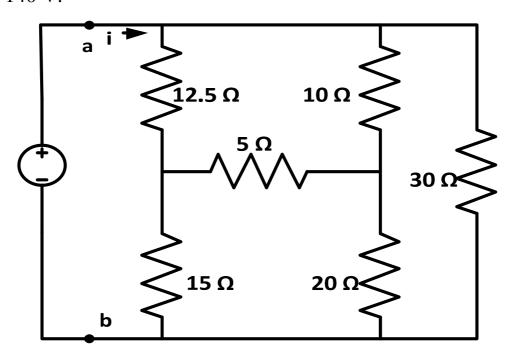
3. a) Obtain the equivalent resistance  $R_{ab}$  between 'a' and 'b' terminals 5M for the circuit shown in Fig. below, by using star-delta transformation technique. Find the current i for the input voltage of 140 V.




b) Derive the expressions of equivalent resistances for converting a star network into a delta network.

(OR)

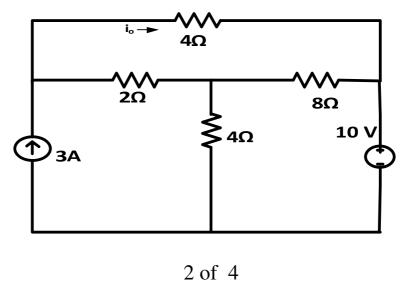4. a) Use mesh analysis to find the current i<sub>o</sub> in the circuit of Fig shown 5M in below.



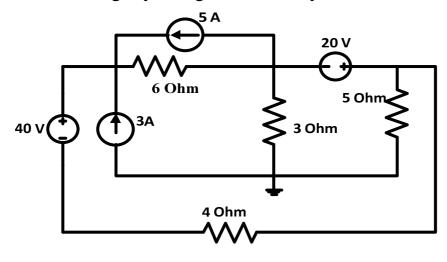b) Determine the power dissipated by  $5\Omega$  resistor for the circuit 5M shown in Fig, by using Nodal Analysis.



**UNIT-III** 

- 5. a) For an alternating waveform, define the following quantities 5M with their units by giving one example.
  - i) Instantaneous value ii) Peak value
  - iii) Average value
- iv) Frequency v) Time period
- b) A coil having a resistance of 7  $\Omega$  in series with an inductance 5M of 31·8 mH is connected to 230 V, 50 Hz supply. Calculate
  - (i) Circuit current
  - (ii) Phase angle
  - (iii) Power factor
  - (iv) Power consumed and
  - (v) Voltage drop across resistor and inductor.

### (OR)

- 6. a) A saw tooth voltage wave increases linearly from 0V to 200 5M V in the interval from 0 to 2 seconds. At t=2 seconds, its value drops to zero suddenly. The waveform repeats this pattern. Find the RMS value and average values of the voltage wave.
  - b) A resistor R in series with a capacitor C is connected to 50 5M Hz, 240V source. Find the value of C so that R absorbs 300W and voltage across R is 100V. Also find the maximum charge and the maximum stored energy in C.

### **UNIT-IV**

7. a) Define the following

4M

- i) Reluctance
- ii) Magneto motive force
- iii) Magnetic field intensity
- b) A circular iron ring has a mean circumference of 1.5 m and a 6M cross-sectional area of 0.01 m<sup>2</sup>. A saw-cut of 4 mm wide is made in the ring. Calculate the magnetizing current required to produce a flux of 0.8 mWb in the air gap if the ring is wound with a coil of 175 turns. Assume relative permeability of iron as 400 and leakage factor 1.25.

### (OR)

8. a) Compare between magnetic and electrical circuits.

4M

b) Derive the Expression for coefficient of coupling,K in 6M magnetic circuits.

### **UNIT-V**

9. Explain construction of DC machine with the help of neat circuit diagram.

### (OR)

- 10. a) Draw and explain the O.C.C internal and external 5M characteristics of DC shunt generator.
  - b) A DC shunt generator has shunt field winding resistance of 5M  $100 \Omega$ . It is supplying a load of 5kW at a voltage of 250V .If its armature resistance is  $0.22\Omega$ , Calculate the induced e.m.f. of DC generator.

### **UNIT-VI**

- 11. a) A four pole DC Motor has lap connected armature winding. 5M The flux per pole is 30 mWb. The number of armature conductors is 250.Whne connected to 230 V DC supply it draws an armature current of 40A.Calculate the back e.m.f. and the speed with which motor is running. Assume armature resistance is  $0.6\Omega$ .
  - b) Explain any one speed control method of a DC motor. 5M

### (OR)

- 12. a) Derive the expression for the electromagnetic torque 5M developed in a DC Motor.
  - b) Write down the applications of DC series, shunt and compound motors. 5M

#### CODE: 20ESI102 SET-1

### ADITYA INSTITUTE OF TECHNOLOGY AND MANAGEMENT, TEKKALI (AUTONOMOUS)

### I B.Tech II Semester Supplementary Examinations, October-2022 PROGRAMMING FOR PROBLEM SOLVING (Common to CE, EEE & ECE)

	(Common to CE, EEE & ECE)	
Time: 3 Hour	Answer ONE Question from each Unit All Questions Carry Equal Marks All parts of the Question must be answered in one place	Iax Marks: 60
	<u>UNIT-I</u>	
1. a)	What is an Algorithm and Write an Algorithm to Calcuthe Area(A) and Perimeter(P) of a Circle?	ılate 4M
b)	What is Operator Precedence and Explain about different types of operators in C.	ent 6M
	(OR)	
2. a) b)	Explain in detail about Program Development Steps. Write about the C Tokens with suitable examples.	5M 5M
	<u>UNIT-II</u>	
•		
3. a)	Write about nested if-else statements with the general f and a flow chart with suitable examples.	Form 5M
b)	Write a C Program which reads three integers and print 2 <sup>nd</sup> largest among them using if-else statements.	ts the 5M
	(OR)	
4. a)	What is Branching? Explain the following.	4M
	i). break ii). continue iii). goto	
b)	Write the general form of the do-while loop. Write a C Program to evaluate the sum of the first n natural numb using the do-while loop.	
	<u>UNIT-III</u>	
<b>5</b> a)	Write shout the declaration and accessing of Two	5N/
5. a)	Write about the declaration and accessing of Two- Dimensional arrays with suitable examples.	5M
b)	Write a C Program for Matrix addition using the arrays ( <b>OR</b> )	5M
6. a)	Explain the following.	4M
b)	<ul><li>i). Call by Value ii). Call by Reference</li><li>Explain Dynamic Memory Allocation with an example</li></ul>	6M

program?

### **UNIT-IV**

7.	a)	Define Function? Explain types of functions.	4M
	b)	Write a C Program to find the GCD using the Non-Recursive Functions.	6M
		(OR)	
8.	a)	Define Recursion? Write a 'C' program to find the factorial	5M
		of a given number using recursion.	
	b)	Write a C Program to Calculate the factorial of a given	5M
		number using	
		Non-Recursion.	
		<u>UNIT-V</u>	
9.	a)	Write about the definition, declaration, and accessing of structure members with suitable examples	6M
	b)		4M
10	۵)	(OR) What are the differences between structure and union? Cive	6M
10.	,	suitable example programs for each structure and union.	
	b)	Write a program to illustrate the method of sending an entire structure as a parameter to a function?	4M
		<u>UNIT-VI</u>	
11.	. a)	Define a file and explain about reading, opening, and closing of a file with examples.	4M
	b)		6M
	0)	them from the file and display even and odd numbers separately.	0111
		(OR)	
12.	a)	Explain about	6M
		i). ftell() ii). fseek() iii)rewind()	01/1
	b)	Write a C program to copy the content from one file to another file	4M

#### **CODE: 18EST101** SET-2

### ADITYA INSTITUTE OF TECHNOLOGY AND MANAGEMENT, TEKKALI (AUTONOMOUS)

I B.Tech II Semester Supplementary Examinations, October, 2022

### BASIC ELECTRICAL ENGINEERING


(Common to CE, CSE, IT Branches)

**Time: 3 Hours** Max Marks: 60


Answer ONE Question from each Unit All Questions Carry Equal Marks All parts of the Question must be answered at one place
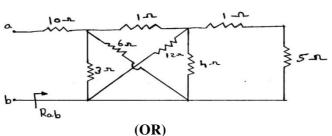
#### **UNIT-I**

- State and explain Kirchhoff Current Law with example. 1. a) 6M 6M
  - Calculate the equivalent resistance  $R_{ab}$  in the circuit. b)



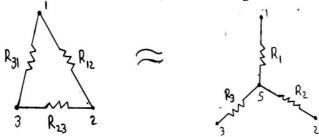2. a) Derive resistance R<sub>1</sub>, R<sub>2</sub>, R<sub>3</sub> to transform given delta network to star network 6M



- Explain the difference between an ideal voltage source and a practical voltage source. b) 6M
  - **UNIT-II**
- Explain RMS and average values of an alternating quantities. 3. a) 6M

6M

6M

6M

Define (i) active power (ii) reactive power and (ii) apparent power b)

(OR)

4. A series circuit consisting of a  $10\Omega$  resistance,  $100 \,\mu f$  capacitance and a  $10 \,m$  H 12M inductance is driven by a 50 Hz ac voltage source of maximum value 100 volts. Calculate (i) the equivalent impedance (ii) current in the circuit and (iii) the power factor of the circuit.

5. With a neat diagram explain about the construction of DC generator. 12M

(OR)

Discuss the various methods of speed control of a D.C motor. 6. 12M

#### **UNIT-IV**

- Derive the emf equation of a single phase transformer. 7. a)
  - Explain how the efficiency of a single phase transformer can be calculated. b)

(OR)

A 500/250V, 10 KVA single phase 50Hz transformer gave the following details 8. 12M OC test(LV side): 250V, 3A, 200W SC test (HV side): 25V, 20A, 300W

Determine the regulation and efficiency at full load and 0.8 lagging power factor.

#### **UNIT-V**

- Derive the torque and power expressions of 3 phase induction motor 9. 12M (OR)
- 10. Illustrate the constructional differences between squirrel cage and slip ring induction 12M motors.

#### **CODE: 18EST102** SET-2

### ADITYA INSTITUTE OF TECHNOLOGY AND MANAGEMENT, TEKKALI (AUTONOMOUS)

I B.Tech II Semester Supplementary Examinations, October, 2022

### PROGRAMMING FOR PROBLEM SOLVING

(Common to EEE, ME Branches)

**Time: 3 Hours** Max Marks: 60

Answer ONE Question from each Unit All Questions Carry Equal Marks All parts of the Question must be answered at one place

### **UNIT-I**

1.	a) b)	Explain about functional block diagram of computer. List the basic data types, their sizes and range of values supported by C Language	6M 6M
	,	$(\mathbf{OR})$	
2.	a)	Discuss about compilation and execution of c program.	6M
	b)	Explain about conditional and relational operator in c	6M
		<u>UNIT-II</u>	
3.	a)	Write a C program to find reverse of a number for eg 123 o/p:321	6M
	b)	Explain about various unconditional statements available in C language with suitable examples.	6M
		(OR)	
4.	a)	Write about switch statement with suitable example	6M
	b)	Explain about various iterative statements available in C language with suitable examples.	6M
		<u>UNIT-III</u>	
5.	a)	Write a C program to find length of a string with and without string handling	6M
		functions	
	b)	Explain how to pass arrays to functions with example.	6M
6.	a)	(OR) Write a C program to perform multiplication of two matrices.	6M
0.	a) b)	What is recursion? Write the difference between iteration and recursion.	6M
		<u>UNIT-IV</u>	
7.	a)	What is pointer? Explain how to initialize a pointer variable. List the advantages of	6M
		pointers.	
	b)	Explain the syntax with suitable examples the dynamic memory allocation functions available in C?	6M
		(OR)	
8.	a)	Differentiate Static memory Allocation and Dynamic Memory Allocation.	6M
	b)	Write a 'C' program to illustrate the use of pointers in arithmetic operations.	6M
		<u>UNIT-V</u>	
9.	a)	Explain the following with examples: fgetc(), fputc(), fscanf()	6M
	b)	Define structure? Write a sample program to demonstrate the structure student. <b>(OR)</b>	6M
10.	a)	Write a program to create a file with some integers and read the numbers from the	6M
	b)	file and display even and odd separately.  Differentiate Structure and Union	6M
	UJ	Differentiate different and Official	OIVI

# CODE: 18ECT103 SET-2 ADITYA INSTITUTE OF TECHNOLOGY AND MANAGEMENT, TEKKALI (AUTONOMOUS)

### I B.Tech II Semester Supplementary Examinations, October, 2022 ELECTRONIC CIRCUITS

(Electronics and Communication Engineering)

Time: 3 Hours Max Marks: 60

Answer ONE Question from each Unit All Questions Carry Equal Marks All parts of the Question must be answered at one place

### **UNIT-I**

- 1. a) Define the following terms in detail (i)ripple factor (ii)peak 6M inverse voltage. (iii)efficiency (iv)transformer utilization factor (v)form factor (vi)peak factor
  - b) In a Half –wave rectifier an AC voltage of peak value 24V is 6M connected in series with a silicon diode and load resistance of  $480\Omega$ , Find the peak current flowing through the diode

### (OR)

- 2. a) Draw the circuit diagram of Half-wave rectifier and derive the 6M expressions for average value, R.M.S value and voltage drop across diode.
  - b) Derive the expression for a ripple factor in a full-wave 6M rectifier with resistive load in detail

### **UNIT-II**

- 3. a) Draw and explain the ripple factor of full-wave rectifier with 6M shunt capacitor filter in detail.
  - b) Give the list of different filters used in rectifier and their merits and demerits.

### (OR)

- 4. a) Explain the working of transistor shunt regulator with neat diagram. 6M
  - b) An L-C filter is to be used to provide a dc output with 1% filter from a full-wave rectifier operating at 50Hz.AssumeL/C =0.01, determine the required values of L and C.

### **UNIT-III**

5. a) Explain how the fixed-bias establishes the stable operating point.

b) For the circuit shown below, determine I<sub>B</sub>, I<sub>C</sub> and V<sub>CE</sub>. 6M  $\beta = 90$ (OR) 6. a) Explain about diode compensation for  $V_{BE}$  and  $I_{CO}$ . 6M b) Define Thermal runaway. Derive the necessary condition to 6M avoid thermal runaway in a transistor? **UNIT-IV** 7. Explain the comparison of low frequency analysis of 12M transistor amplifier configurations. (OR) 8. a) Give the advantages of H-parameter analysis. 6M Explain in detail about the h-parameters using a two port 6M network model. **UNIT-V** Show that bandwidth increases in negative feedback 9. 6M a) amplifiers. An amplifier has an input resistance of 200 K $\Omega$ , with certain 6M negative feedback introduced in the above amplifier the input resistance is found to be 20 M $\Omega$  and overall gain is found to be 1000. Calculate the loop gain and feedback factor. (OR) 10. a) Draw the circuit of a voltage series feedback amplifier and 6M derive the expressions for Rif and Rof. b) Draw the block diagrams of four types of negative feedback 6M amplifier circuits and explain the advantages and

disadvantages.

### **CODE: 16EE1004**

### ADITYA INSTITUTE OF TECHNOLOGY AND MANAGEMENT, TEKKALI (AUTONOMOUS)

I B.Tech II Semester Supplementary Examinations, October, 2022

### BASIC ELECTRICAL & ELECTRONICS ENGINEERING (Common to CE & ME branches)

Max Marks: 70 **Time: 3 Hours** 


> Answer ONE Question from each Unit All Questions Carry Equal Marks All parts of the Question must be answered at one place

### **UNIT-I**

List the basic network elements? Write their volt-ampere relationship. 1. a. 7MTwo resistors of  $40\Omega$  and  $60 \Omega$  in parallel are connected in series with two  $0.5\Omega$  resistors. 7M b. Find the voltage across the series resistors and across the parallel resistors when 125 volt is applied to the entire circuit.

(OR)

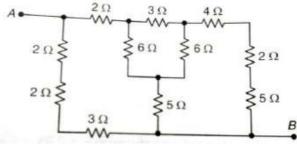2. Calculate the effective resistance between the points A and B in the circuit shown in 7Mfigure.



b. Explain how the current is divided in a parallel circuit? 7M

### **UNIT-II**

Discuss the constructional details of DC Generator 3. a.

7M 7M

A long-shunt compound generator delivers a load current of 50A at 500V and has b. armature, series field and shunt field resistances of  $0.05 \Omega$ ,  $0.03\Omega$  and  $250\Omega$  respectively. Calculate the generated voltage and the armature current. Allow 1 V per brush for contact drop.

(OR)

Derive the torque equation for d.c.motor. 4. a.

7M

A 6 pole wave wound dc generator is having 50 slots with 25 conductors per slot and b. rotating at 1500 rpm. The flux per pole is 0.015 wb, calculate the emf generated?

7M

#### **UNIT-III**

5. Derive the E.M.F equation of Transformer a.

7M

Explain how efficiency and regulation of a transformer are determined? b. (OR)

7M

Discuss the principle of operation of induction motor. 6. a.

7M

Derive the torque equation for a induction motor. b.

7M

#### **UNIT-IV**

7. With a neat diagram explain the principle operation of alternator? a.

7M 7M

Derive the EMF equation of an alternator? b.

(OR) Explain the working of Repulsion type Moving iron Instrument 8. a. List the merits and demerits of PMMC instruments?

7M 7M

#### **UNIT-V**

Explain the working of full-wave rectifier with neat waveforms 9. a. b.

7M

Differentiate between NPN and PNP junction transistors?

7M

- (OR)
- 10. Explain the construction and working of P-N junction diode with a neat diagram a.

7M

Explain the working of a PNP transistor b.

b.

## CODE: 16CS1001 SET-1 ADITYA INSTITUTE OF TECHNOLOGY AND MANAGEMENT, TEKKALI

(AUTONOMOUS)

### I B.Tech II Semester Supplementary Examinations, October-2022

### **COMPUTER PROGRAMMING**

(Common to EEE & ECE)

Time: 3 Hours Max Marks: 70

Answer ONE Question from each Unit All Questions Carry Equal Marks All parts of the Question must be answered at one place

### **UNIT-I**

1.	a) b)	Write an algorithm and draw flowchart to find greatest among three given numbers. Explain about logical and bitwise operators with suitable examples.  (OR)	7M 7M	
2.	a) b)	Define flow chart .Explain program development steps with neat diagram.  Discuss about the structure of a C program with necessary steps and diagram/	7M 7M	
		<u>UNIT-II</u>		
3.	a)	Define switch case statement. Write a program to find grades of n number of students using switch case.	7M	
	b)	Write a program to print n Fibonacci numbers using while statement.  (OR)	7M	
4.	a) b)	Write syntax and structure of i) ifelse ii) if ladder and discuss with examples. Write a program using for loop to find greatest of n numbers.	7M 7M	
		<u>UNIT-III</u>		
5.	a) b)	Define array. How to access array elements? Explain.  Describe about storage classes in C.	7M 7M	
6.	a)	(OR) Explain about double dimensional array and write a program to find addition of 2 matrices.	7M	
	b)	What is the difference between call by value and call by reference? Discuss the problems associated with them.	7M	
		<u>UNIT-IV</u>		
7.	a)	Write the procedure for swapping of two strings using pointers.	7M	
	b)	Describe the process of deflation and, initializing a union with an example.  (OR)	7M	
8.	a)	Describe the two ways of accessing a structure member through a pointer. Explain the same with an example.	7M	
	b)	What is structure? Explain array of structures with example.	7M	
<u>UNIT-V</u>				
9.	a)	Explain about the functions for reading and writing data from a file.	7M	
	b)	Write a C program to count the number of characters and number of lines in a file. (OR)	7M	
10.	a) b)	Describe the process of handling errors during file operations.  Write a C program to print file contents in reverse order.	7M 7M	