

**BASIC ELECTRICAL ENGINEERING  
(Common to EEE, ME, ECE Branches)**

**Time: 3 Hours**

**Max Marks: 60**

Answer ONE Question from each Unit

All Questions Carry Equal Marks

All parts of the Question must be answered at one place

**UNIT-I**

1 a) State and explain Kirchoff's laws. [8M]

b) Determine voltage across A and B for the circuit shown in figure.1 [4M]

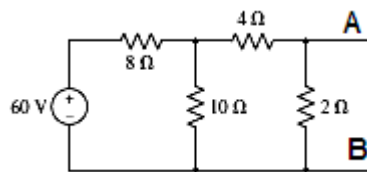


Figure.1

**OR**

2.a) Using  $\Delta$ -Y or Y- $\Delta$  conversion, find the current I in the circuit shown in figure 2? [6M]

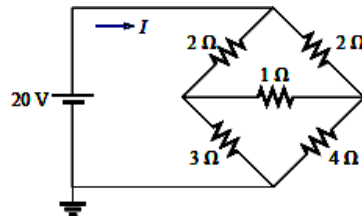


Figure.2

b) Find the equivalent resistance  $R_{ab}$  in the circuit shown in figure.3 [6M]

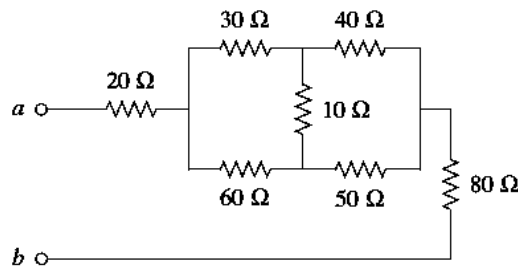


Figure.3

## UNIT-II

- 3.a) Define the following with respect to sinusoidal quantity: [4M]  
i) RMS Value ii) Average Value iii) Form factor iv) Peak factor.  
b) A coil has a resistance of  $4\ \Omega$  and an inductance of  $9.55\text{ mH}$ . Calculate (i) the reactance, (ii) the impedance, and (iii) the current taken from a  $240\text{V}$ ,  $50\text{ Hz}$  supply. Determine also the phase angle between the supply voltage and current. [8M]

**OR**

4. Determine the average value, rms value and form factor of the current waveform in figure.4 [12M]

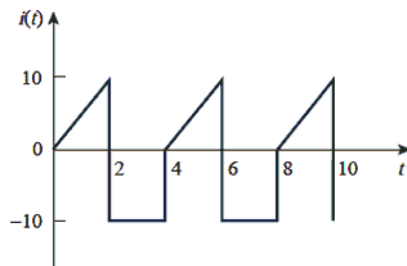


Figure.4

## UNIT-III

5. Explain the OCC, Internal and External characteristics of Dc shunt Generator? [12M]  
**OR**  
6. Explain the working of 3- point starter with neat diagram. [12M]

## UNIT-IV

7. a) Explain about various losses of Single phase transformer? How to minimize them? [6M]  
b) Explain the working principle of a single phase transformer [6M]

**OR**

- 8 a) Briefly explain OC and SC tests performed on transformer with suitable circuit diagrams.? [8M]  
b) A single-phase transformer is rated at  $40\text{ kVA}$ . The transformer has full-load copper losses of  $800\text{W}$  and iron losses of  $500\text{W}$ . Determine the transformer efficiency at full load,  $75\%$  of load and  $0.8$  power factor. [4M]

## UNIT-V

- 9 a) Explain the operating principle of Three phase Induction motor.? [8M]  
b) The stator of a 3-phase, 4-pole induction motor is connected to a  $50\text{ Hz}$  supply. The rotor runs at  $1455\text{ rev/min}$  at full load. Determine (i) the synchronous speed and (ii) the slip at full load. [4M]

**OR**

- 10 a) Derive the torque equation of induction motor. [6M]  
b) A three-phase induction motor runs at  $1440\text{ rpm}$  at full load when supplied power from  $50\text{ Hz}$ , 3-phase line. Calculate i) slip at full load ii) frequency of rotor voltage iii) speed of rotor at a slip of  $10\%$ . [6M]