

**Time: 3 Hours****Max Marks: 60**


Answer ONE Question from each Unit

All Questions Carry Equal Marks


All parts of the Question must be answered at one place

**UNIT-I**

1. a) State and explain Kirchhoff's laws 4M
- b) Solve the network shown in Fig, for the current in the  $8\Omega$  resistor by using Kirchhoff's laws. 8M

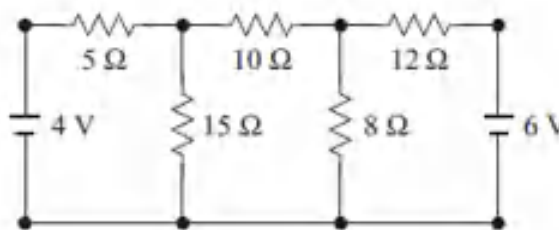**(OR)**

2. a) Explain about Star-Delta transformation with example. 6M
- b) Find the equivalent resistance as viewed through the terminals 6M
  - i) B and C ii) A and N

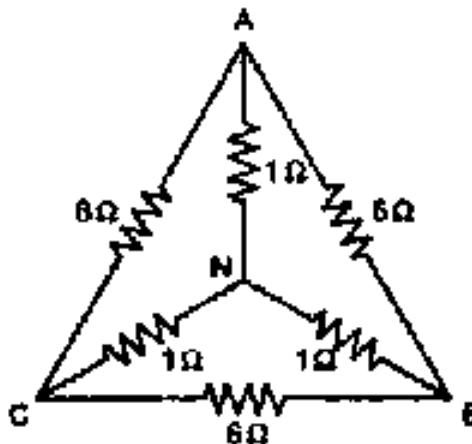**UNIT-II**

3. a) Determine current passing through RL series circuit for supply voltage of  $v = v_m \sin \omega t$  using sinusoidal analysis and also draw phasor diagrams. 12M

**(OR)**

4. a) Define i) RMS value ii) average value iii) form factor 6M  
 b) Determine Average value, RMS value and Form factor for the sinusoidal waveform. 6M

### **UNIT-III**

5. a) Derive EMF equation of a DC generator. 6M  
 b) A 6-pole lap wound DC generator has 600 conductors on its armature. The flux per pole is 0.02 wb. Calculate (i) the speed at which the generator must run to generate 300W (ii) What would the speed if it is wave wound 6M

**(OR)**

6. a) Explain the working of three point starter with neat sketch? 6M  
 b) A 4-pole, 250V dc shunt motor has a lap connected armature with 960 conductors. The flux per pole is 20mwb. Calculate the torque developed by the armature and the useful torque when the current taken by the motor is 30A. The armature resistance is  $0.12\Omega$  and the field resistance is  $125\Omega$ . The mechanical and iron losses are 825W. 6M

### **UNIT-IV**

7. a) Explain how the maximum efficiency of a transformer can be predicted from the results of OC and SC test results. 6M  
 b) A 5KVA, 2000/250V, 1- $\Phi$  Transformer gave the following test results 6M  
 O.C TEST: 250V, 0.8A, 50W (L.V SIDE)  
 S.C TEST: 60V, 3A, 45W (H.V SIDE).  
 Calculate the efficiency at full load and half load at 0.8 power factor lagging?

**(OR)**

8. a) Derive the EMF equation of a 1- $\phi$  transformer. 6M  
 b) Explain open circuit and short circuit tests for a single phase transformer. 6M

### **UNIT-V**

9. a) Explain the types of rotors in 3 phase induction motor. 6M  
 b) A 3 phase, 6 pole 50HZ induction motor develops 3.73KW at 960r.p.m. what will be the stator input if the stator loss is 240W. 6M

**(OR)**

10. a) Draw and explain the Speed-Torque Characteristics? 6M  
 b) The power input to a 4-pole, 3-phase, 50HZ motor is 52KW; the speed is 14600r.p.m. the stator losses are 1.6KW and the friction and windage losses are 2KW. Find the slip, the rotor copper losses and the efficiency. 6M

# AR16

CODE: 16EE1001

SET-2

ADITYA INSTITUTE OF TECHNOLOGY AND MANAGEMENT, TEKKALI  
(AUTONOMOUS)

I B.Tech I Semester Supplementary Examinations, Oct / November-2021

BASIC ELECTRIC CIRCUIT ANALYSIS

(Electrical and Electronics Engineering)

Time: 3 Hours

Max Marks: 70


Answer ONE Question from each Unit

All Questions Carry Equal Marks

All parts of the Question must be answered at one place


## UNIT-I

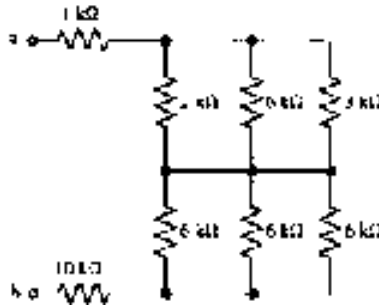1. a) Explain independent and dependent sources in brief 7M
- b) Find  $R_{ab}$  in fig. shown below. 7M




(OR)

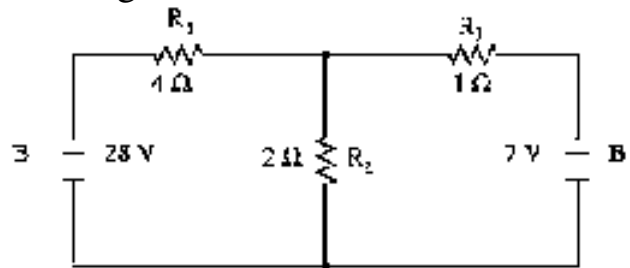2. a) Explain KCL and KVL in brief. 7M
- b) Find current through each resistor. 7M




## UNIT-II

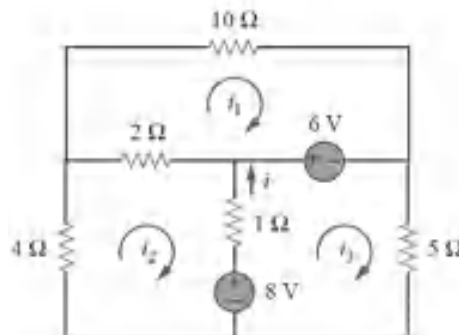3. a) Find  $i_1$   $i_2$   $i_3$  in fig shown below. 7M




b) Find  $i_1$ ,  $i_2$  in fig shown below.

7M

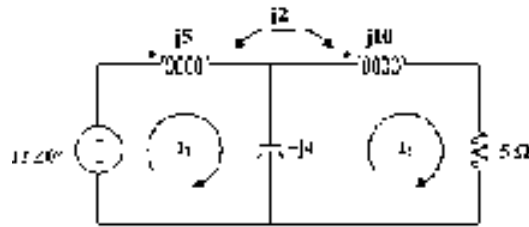

(OR)

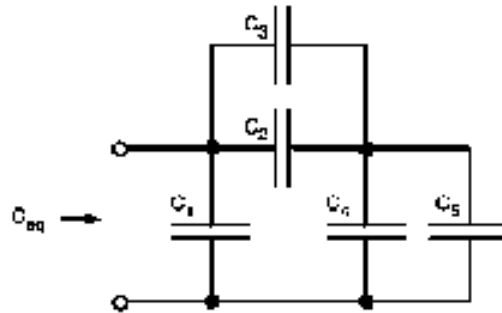4. a) Find  $C_{eq}$  in fig. shown below. Each capacitance value is  $2\mu F$ . 4M




b) i) Explain Faraday laws of Electromagnetic Induction. 6M

ii) Define a) self induced emf b) mutual induced emf 4M

### UNIT-III

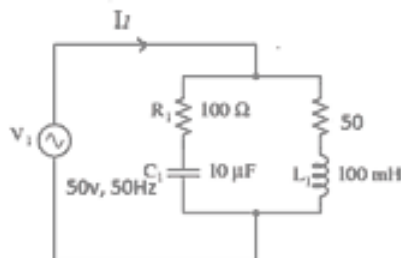5. a) Find  $I_1$  in fig. shown below. 6M




b) Define i) form factor ii) peak factor iii) cycle iv) 8M

Admittance

(OR)

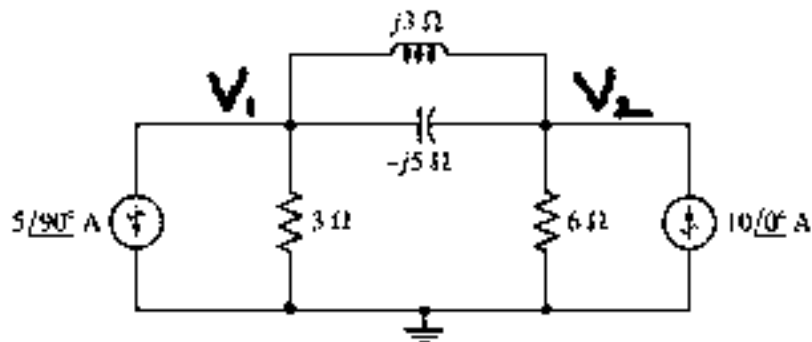
6. a) Find  $V_1$  and  $V_2$  in fig. shown below. 7M



- b) Define i) RMS value ii) Average value iii) frequency iv) power factor of an alternating quantity. 7M

### UNIT-IV

7. a) Find I in fig. shown below. 7M

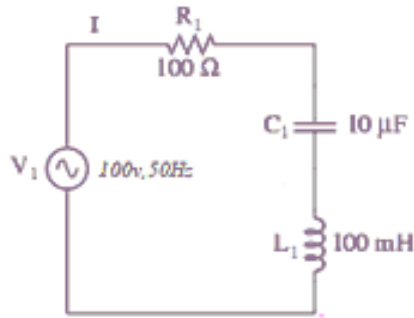


- b) Write the differences between series and parallel resonances 7M

(OR)

8. a) A series RLC circuit consist of a  $50\Omega$  resistance ,0.2H inductance and  $10\mu\text{F}$  capacitor with an applied voltage of 20V. Determine the resonant frequency. Find the Q factor of the circuit. Compute the lower and upper frequency limit and also find the bandwidth of the circuit 7M

- b) Find I in fig. shown below. 7M

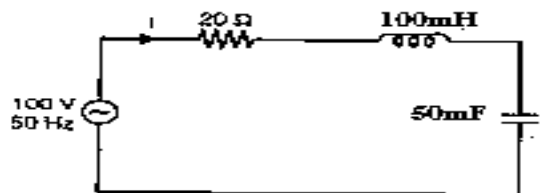

### UNIT-V

9. a) Draw the phasor diagram for a balanced Star-connected supply system and establish the relation between line voltages and phase voltages. 7M

- b) The phase voltage of a star connected 3 phase AC generator is 230 volts. calculate the(i) line voltage (ii) active power output if the line current of the system is 15A the power factor of 0.7 and (iii) active power and reactive power components of the phase current 7M

**(OR)**

10. a) Three impedances of  $(7+4j) \Omega$ ,  $(3+2j) \Omega$  and  $(9+2j) \Omega$  are connected between neutral and the red, yellow and blue phases respectively of a three phase four wire system, the line voltage is 440 volt. Calculate i) the current in the each line and ii) the current in the neutral wire. 7M
- b) Briefly explain 3-phase unbalanced power using two wattmeter method 7M

# AR16

**CODE: 16EE1002**

**SET-2**

**ADITYA INSTITUTE OF TECHNOLOGY AND MANAGEMENT, TEKKALI  
(AUTONOMOUS)**

**I B.Tech I Semester Supplementary Examinations, Oct / November-2021**

## **NETWORK ANALYSIS**

**(Electronics & Communication Engineering)**

**Time: 3 Hours**

**Max Marks: 70**


Answer ONE Question from each Unit

All Questions Carry Equal Marks

All parts of the Question must be answered at one place


### **UNIT-I**

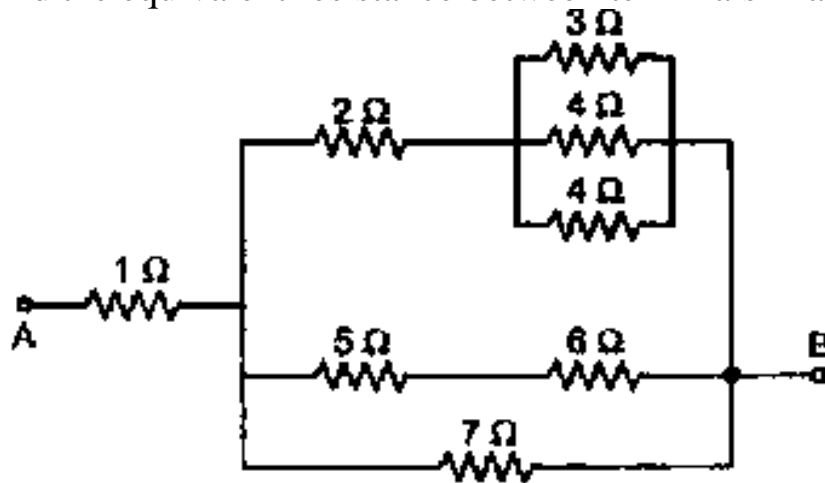1. a) Explain in brief elements of electrical network. 8M
- b) Find the equivalent resistance between terminals A and B 6M



**(OR)**

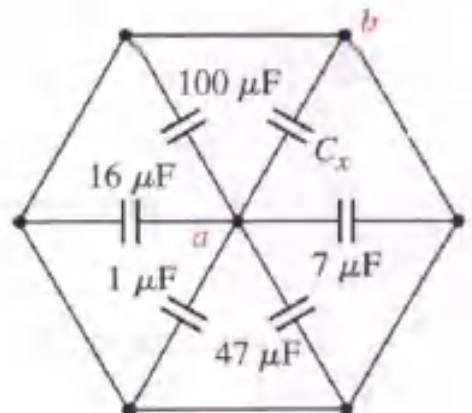
2. a) The network of figure stores 534.8 micro Joules of energy when a voltage of 2.5V is connected to terminals a and b, what is the value of  $C_x$ ? 8M



- b) Discuss about voltage and current division rules. 6M


## UNIT-II

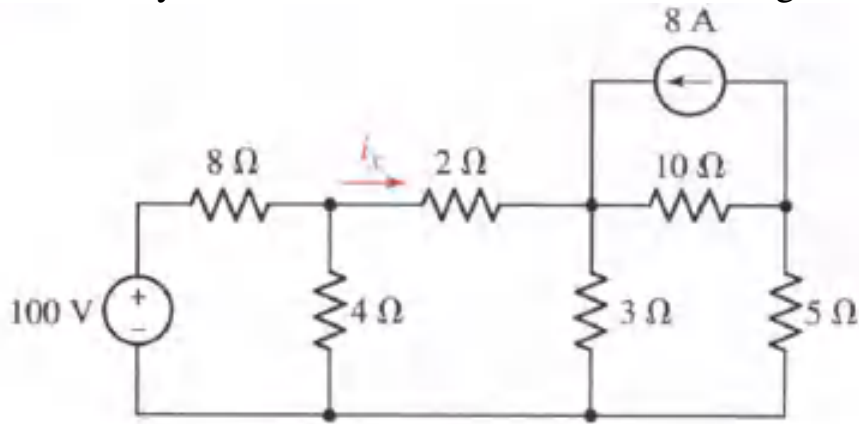3. a) Explain in brief Kirchhoff's laws 6M  
 b) Use mesh analysis to find  $i_x$  in the circuit shown in figure 8M




(OR)

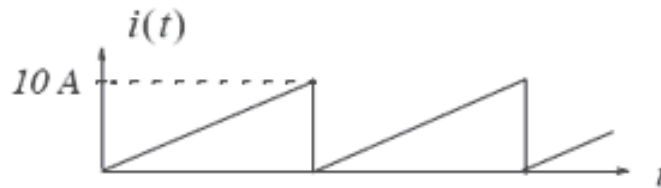4. a) Compute the  $I_{avg}$  and  $I_{rms}$  for the saw-tooth waveform shown in Figure 7M  
 in Figure



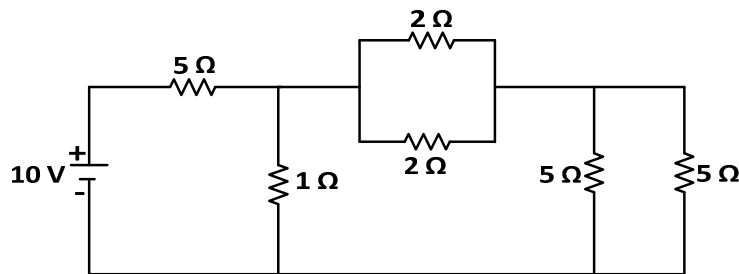
- b) Use series and parallel reduction technique and find the Power delivered by the source . 7M





### UNIT-III

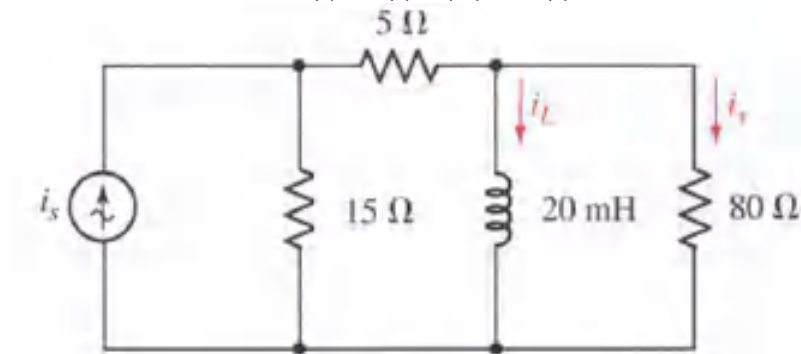5. a) Define impedance, admittance, reactance and conductance. 6M  
b) If  $i_s = 0.4 \cos 500t$  A in the circuit shown in figure, simplify the circuit and then find (i)  $i_L(t)$ ; (ii)  $i_X(t)$ . 8M




(OR)

6. Obtain the resonant frequency and quality factor and bandwidth for a parallel RLC circuit. 14M

### UNIT-IV

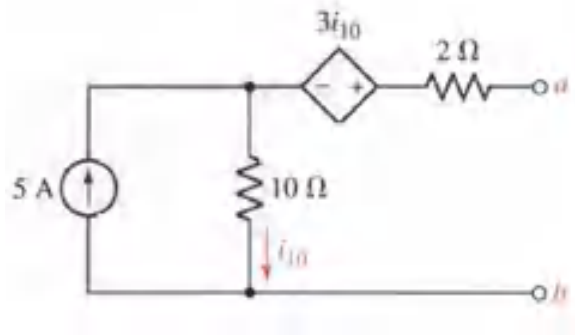7. a) State and explain Superposition theorem with suitable example 7M  
b) State and explain Thevenin's theorem with suitable example 7M  
(OR)  
8. a) State and explain Reciprocity theorem with suitable example 6M  
b) Find the Maximum power that could drawn from source 8M




## UNIT-V

9. a) Obtain Z parameters in terms of Y parameters 7M  
b) Obtain ABCD parameters in terms of Z parameters 7M

(OR)

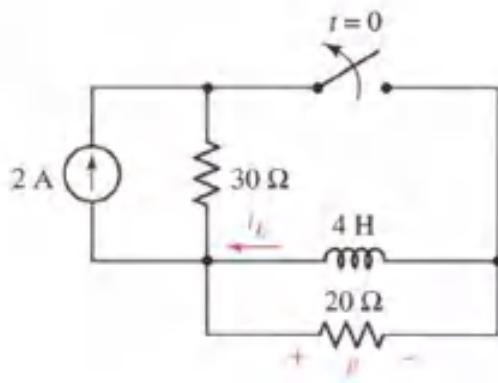10. a) The switch in the circuit of figure has been closed since a long time. If the switch is opened at  $t=0$ , find (i)  $i_L$  the instant after the switch changes. 7M



- b) Explain in brief the response of RLC series circuit 7M

4 of 4

\*\*\*

# AR16

**CODE: 16EE1003**

**SET-2**

**ADITYA INSTITUTE OF TECHNOLOGY AND MANAGEMENT, TEKKALI  
(AUTONOMOUS)**

**I B.Tech I Semester Supplementary Examinations, Oct / November-2021**

**ELECTRICAL AND ELECTRONICS ENGINEERING**

**(Common to CSE, IT Branches)**

**Time: 3 Hours**

**Max Marks: 70**

Answer ONE Question from each Unit

All Questions Carry Equal Marks

All parts of the Question must be answered at one place

## **UNIT-I**

1. Compute the necessary equations for delta to star connection when the resistors  $R_1, R_2, R_3$  are connected in delta. 14M

**(OR)**

2. a) Derive the expression for energy stored in capacitor? 7M  
b) (i) Find the value of an inductor which carries 2 A. of current and in which 20 J of energy is stored. 7M  
(ii) Find the value of a capacitor with 500 volts across it, in which 20 J of energy is stored.

## **UNIT-II**

3. Discuss various speed control methods of a DC motor? 14M

**(OR)**

4. a) A four-pole generator has 500 conductors on the armature. If the generator is running at 1200 rpm, find the average voltage generated between brushes for (a) a lap winding, (b) a wave winding. The total flux per pole is  $10^6$  lines. 7M  
b) Explain the operation of 3-point starter? 7M

## **UNIT-III**

5. a) An induction motor draws 25 A from a 460-V, three-phase line at a power factor of 0.85, lagging. The stator copper loss is 1000 W, and the rotor copper loss is 500 W. The "rotational" losses are friction and windage = 250 W, core loss = 800 W, and stray load loss = 200 W. Calculate  
(i) the air-gap power,  $P_g$ ,  
(ii) the developed mechanical power, DMP,  
(iii) the output horsepower, and (iv) the efficiency. 7M  
b) Discuss about Open circuit tests in single phase transformer? 7M

**(OR)**

6. a) Discuss the parameters of single phase transformers: 7M  
       i. Efficiency ii. Voltage regulation  
 b) Explain torque-speed characteristics of three phase induction motor? 7M

### UNIT-IV

7. Explain the principle of operation of alternator and derive its EMF equation? 14M

(OR)

8. Explain briefly the construction and operation of Moving Coil instruments? 14M

### UNIT-V

9. a) Explain the operation of Center tapped rectifier with neat diagrams? 7M  
 b) For the half-wave rectifier circuit shown, determine 7M  
       (i)  $I_{dc}$ ,  
       (ii)  $I_{rms}$ ,  
       (iii) the ripple factor  $r$ ,  
       (iv) the rectifier efficiency  
       (v) the peak inverse voltage PIV.



(OR)

10. a) Explain P-N junction diode and its V-I characteristics with neat diagram? 7M  
 b) Discuss the modes of operation of N-P-N transistor? 7M

# AR16

**CODE: 16EE1004**

**SET-1**

**ADITYA INSTITUTE OF TECHNOLOGY AND MANAGEMENT, TEKKALI  
(AUTONOMOUS)**

**I B.Tech II Semester Supplementary Examinations, Oct / November-2021**

**BASIC ELECTRICAL & ELECTRONICS ENGINEERING**

**(Common to CE & ME branches)**

**Time: 3 Hours**

**Max Marks: 70**

Answer ONE Question from each Unit

All Questions Carry Equal Marks

All parts of the Question must be answered at one place

## **UNIT-I**

1. a) State Kirchhoff's current and voltage laws. Explain with suitable examples. 7M
  - b) Derive the expressions for converting a Delta network to a Star network. 7M
- (OR)**
2. a) Write the brief notes on V-I relationships for the following elements  
i) Inductor 6M  
ii) capacitor.
  - b) Derive the expression for parallel RLC circuit to determine voltage drop across each element. 8M

## **UNIT-II**

3. a) Derive an E.M.F. equation of D.C Generator. 7M
  - b) Classify the D.C. generators, Draw and explain external characteristics of D.C. shunt generator. 7M
- (OR)**
4. a) Explain any one of the speed control methods of D.C. shunt motor. 8M
  - b) A 4-pole motor is fed at 440v and takes an armature current of 50A. The resistance of the armature circuit is 0.28 ohms. The armature is wave-wound with 888 conductors and the useful flux per pole is 0.023Wb. Calculate the speed. 6M

### **UNIT-III**

5. a) Explain the principle and operation of 3-Phase Induction motor with neat diagram. 7M  
b) Derive an E.M.F. equations of single phase transformer. 7M

**(OR)**

6. a) Discuss the procedure for implementing OC and SC tests on a single phase transformer. How the parameters can be found from these tests? 8M  
b) Compare 3-phase induction motors and determine the synchronous speed and slip of a 6pole, 3-phase, 50Hz induction motor. 6M

### **UNIT-IV**

7. a) Explain the principle and operation of an alternator with neat diagram. 7M  
b) Explain the procedure to find the regulation of alternator by synchronous impedance method. 7M

**(OR)**

8. a) Explain the different torques in measuring instruments. 8M  
b) Explain the principle operation of attraction type moving iron instrument with neat diagram and mention its advantages. 6M

### **UNIT-V**

9. a) Explain the working and operation of full wave rectifier and draw the output wave forms. 8M  
b) Explain the working of transistor and draw the symbols of P-N-P and N-P-N transistor. 6M

**(OR)**

10. a) Explain the working of P-N junction diode and its applications. 6M  
b) A half wave rectifier has a load of  $3.5 \text{ k}\Omega$ . If the diode resistance and secondary coil resistance together has a resistance of  $800 \text{ }\Omega$ . The input voltage has a single voltage of peak value  $240\text{V}$ . Calculate i) Peak, average and RMS value of current flowing ii) D.C. power output iii) A.C. power input and iv) efficiency of the rectifier. 8M

# AR13

CODE: 13EE1002

SET-2

ADITYA INSTITUTE OF TECHNOLOGY AND MANAGEMENT, TEKKALI  
(AUTONOMOUS)

I B.Tech II Semester Supplementary Examinations, Oct / November-2021

BASIC ELECTRICAL AND ELECTRONICS ENGINEERING

(Common to MECH & CIVIL Branches)

Time: 3 Hours

Max Marks: 70

## PART-A

ANSWER ALL QUESTIONS

[1 x 10 = 10 M]

1. a) V-I relation of R, L, C.  
b) Voltage division formula.  
c) Applications of DC Shunt Generator.  
d) Types of DC Motors.  
e) Equation for slip of a 3-phase induction motor.  
f) Condition for maximum efficiency of a transformer.  
g) Define voltage regulation of a transformer.  
h) Mention the three torques in an indicating instrument.  
i) Characteristics of a diode.  
j) Output wave form of a half wave rectified wave.

## PART-B

Answer one question from each unit


[5x12=60M]

### UNIT-I

2. a) Explain Kirchhoff's laws with suitable examples.  
b) Find current and voltage across each resistor.

6 M

6 M

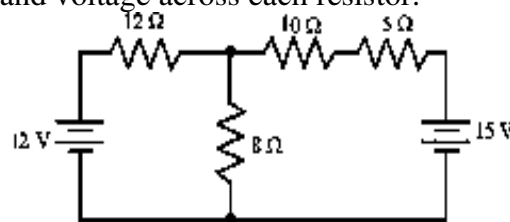


(OR)

3. a) Explain about current division and voltage division. Where do you use them?  
b) Find  $R_{eq}$  for the circuit.

6 M

6 M

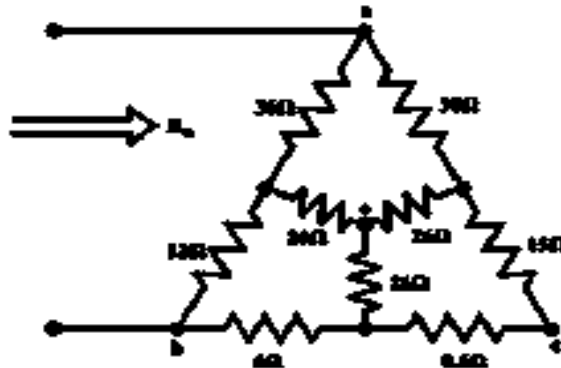

## **UNIT-II**

4. a) Derive the equation for the efficiency of a DC Machine. **6 M**  
b) What is the necessity of a starter? Explain three point starter with a neat diagram. **6 M**

**(OR)**

5. a) Derive the EMF equation of DC generator. **6 M**  
b) Explain any one of the speed control methods of a DC Motor. **6 M**

## **UNIT-III**

6. a) Derive the emf equation of an alternator. **6 M**  
b) What are the various parts of an induction motor? Explain in detail. **6 M**

**(OR)**

7. a) How do you determine the efficiency of a transformer? **6 M**  
b) How a rotating magnetic field is produced in 3-phase induction motor? **6 M**

## **UNIT-IV**

8. What are the types of measuring instruments? Explain about any one type. **12 M**

**(OR)**

9. a) What are the different torques needed for an indicating instrument? **6 M**  
b) How do you increase the range of a volt meter? **6 M**

## **UNIT-V**

10. a) Explain about full wave rectifier. Also draw its waveform. **6 M**  
b) Diode Characteristics and Applications. **6 M**

**(OR)**

11. a) Explain the operation of PNP transistor. Draw its characteristics. **6 M**  
b) Write about SCR. **6 M**